

## DIGITAL LOGIC SYSTEMS : ASSIGNMENT 7

AAKASH JOG  
ID : 989323563  
&  
DUSTIN CHALCHINSKY  
ID : 209741891  
&  
PAUL MIERAU  
ID : 932384233

### Exercise 1.

Design a combinational circuit that implements the following specification.

Input  $X[2^k - 1 : 0] \in \{0, 1\}^{2^k}$

Output  $L, R \in \{0, 1\}^k$

Functionality  $wt(X) = 2 \implies X[\langle L \rangle] = X[\langle R \rangle] = 1$

### Solution 1.

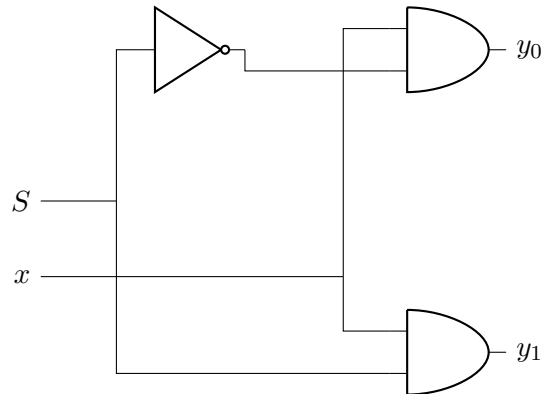


FIGURE 1. DEMUX

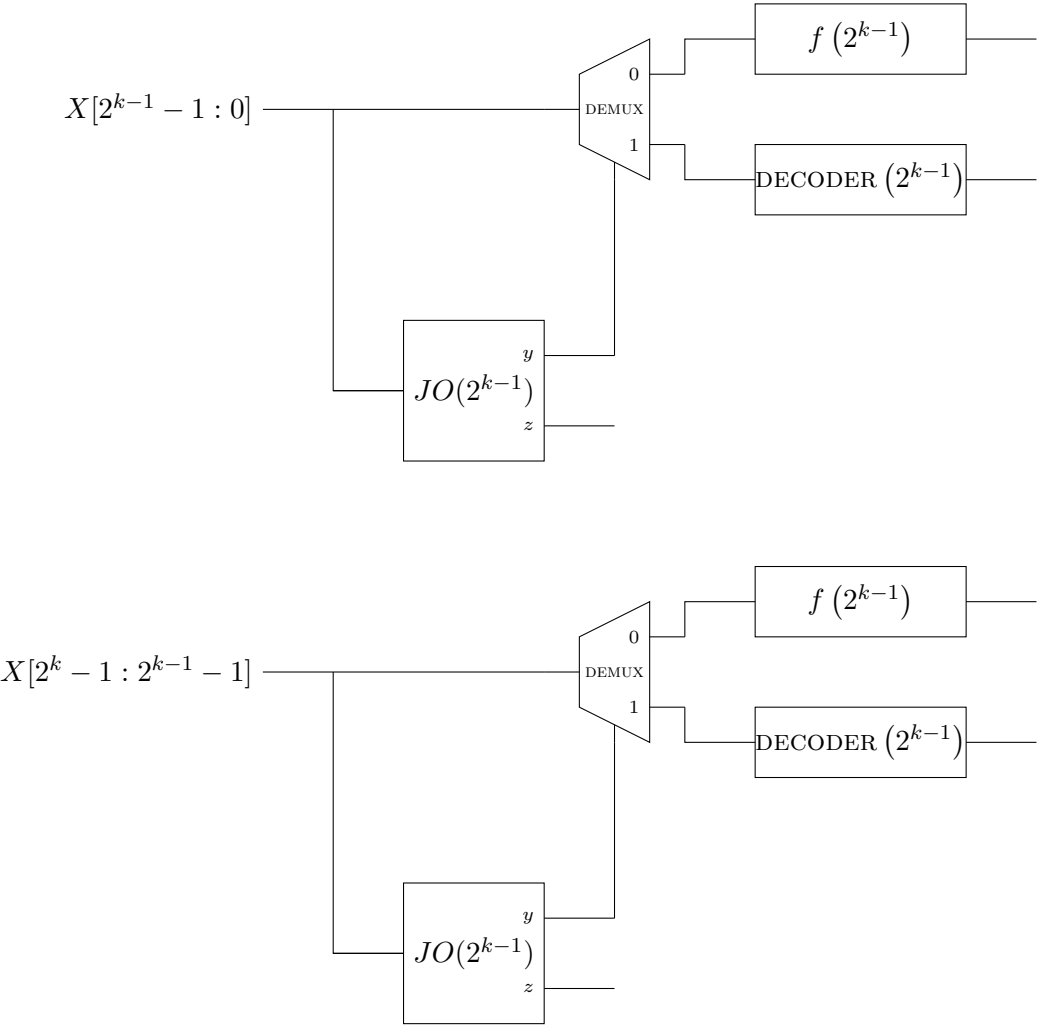


FIGURE 2.  $f(2^k)$